


**Problem Statement:**

- Given Wallace multiplier algorithm implement it using Verilog.
- Implement the algorithm with 8bit x 8bit multiplication.
- Using structural blocks such as Half Adder and Full Adder.
- Generate RTL view.
- Write a Testbench for multiplying various two 8-bit numbers.
- Show two 8-bit multiplication in Modelsim.

**Solution:**

We have implemented a two 8-bit modified wallace multiplier which does not have any redundant Carry bit which it used to occur in normal wallace multiplier.

 **Given below is the modified Wallace Multiplier Algorithm:**



Here in the first layer each dot represents a product between two 1-bit multiplication – for example → for numbers A&B → a7a6a5a4a3a2a1a0 \* b7b6b5b4b3b2b1b0 → one dot = b0a0, b1a1, etc.

For implementing this algorithm, we have used **39 Full Adders and 17 Half Adders**.


Below are code snippets and their respective RTL views of various structural blocks used for generating this algorithm.

For Half Adder:

CODE SNIPPET:

```
module Half_adder(input a,b,  
  output reg sum_h,cout_h);  
  
  always@(*)  
begin  
  sum_h<= a^b;  
  cout_h<= a&b;  
end  
endmodule
```

RTL VIEW:

 


For Full Adder:

CODE SNIPPET:

```
1 module full_adder(input a,b,cin,  
2   output reg sum_f,cout_f);  
3   always@(*)  
4   begin  
5       sum_f <= a^b^cin;  
6       cout_f <= ((a&b)|(b&cin)|(a&cin));  
7   end  
8   endmodule  
9
```

RTL VIEW:

 

**FOR FULL WALLACE MULTIPLIER:**

**CODE SNIPPET:**

```

module wallace_8(input [7:0]a,b,
  output reg [15:0]product);

  wire h[16:0],f[38:0],fc[38:0],hc[16:0];
  reg pp[7:0][7:0];
  integer i,j;

  always@(*)

begin
  for(i=0;i<=7;i=i+1)
    for (j=0;j<=7;j=j+1)
      pp[i][j]<=(a[j]&b[i]);
  end

  // first level

  Half_adder H1(pp[0][1],pp[1][0],h[0],hc[0]);
  full_adder F1(pp[0][2],pp[1][1],pp[2][0],f[0],fc[0]);
  full_adder F2(pp[0][3],pp[1][2],pp[2][1],f[1],fc[1]);
  full_adder F3(pp[0][4],pp[1][3],pp[2][2],f[2],fc[2]);
  full_adder F4(pp[0][5],pp[1][4],pp[2][3],f[3],fc[3]);
  full_adder F5(pp[3][2],pp[4][1],pp[5][0],f[4],fc[4]);
  full_adder F6(pp[0][6],pp[1][5],pp[2][4],f[5],fc[5]);
  full_adder F7(pp[3][3],pp[4][2],pp[5][1],f[6],fc[6]);
  full_adder F8(pp[0][7],pp[1][6],pp[2][5],f[7],fc[7]);
  full_adder F9(pp[3][4],pp[4][3],pp[5][2],f[8],fc[8]);
  full_adder F10(pp[1][7],pp[2][6],pp[3][5],f[9],fc[9]);
  full_adder F11(pp[4][4],pp[5][3],pp[6][2],f[10],fc[10]);
  full_adder F12(pp[2][7],pp[3][6],pp[4][5],f[11],fc[11]);
  full_adder F13(pp[5][4],pp[6][3],pp[7][2],f[12],fc[12]);
  full_adder F14(pp[3][7],pp[4][6],pp[5][5],f[13],fc[13]);
  full_adder F15(pp[4][7],pp[5][6],pp[6][5],f[14],fc[14]);
  full_adder F16(pp[5][7],pp[6][6],pp[7][5],f[15],fc[15]);

  //second level

  Half_adder H2(f[0],hc[0],h[1],hc[1]);
  full_adder F17(f[1],fc[0],pp[3][0],f[16],fc[16]);
  full_adder F18(f[2],fc[1],pp[3][1],f[17],fc[17]);
  full_adder F19(f[3],f[4],fc[2],f[18],fc[18]);
  full_adder F20(f[5],f[6],fc[3],f[19],fc[19]);
  full_adder F21(f[7],f[8],fc[5],f[20],fc[20]);
  full_adder F22(fc[6],pp[6][1],pp[7][0],f[21],fc[21]);

```

```

full_adder F23(f[9], f[10], fc[7], f[22], fc[22]);
half_adder H3(fc[8], pp[7][1], h[2], hc[2]);
full_adder F24(f[11], f[12], fc[9], f[23], fc[23]);
full_adder F25(f[13], fc[11], fc[12], f[24], fc[24]);
full_adder F26(f[14], fc[13], pp[7][4], f[25], fc[25]);
full_adder F27(pp[6][7], pp[7][6], fc[15], f[26], fc[26]);

//third level
half_adder H4(f[16], hc[1], h[3], hc[3]);
full_adder F28(f[17], fc[16], pp[4][0], f[27], fc[27]);
full_adder F29(f[19], fc[18], fc[4], f[28], fc[28]);
full_adder F30(f[20], f[21], fc[19], f[29], fc[29]);
full_adder F31(f[22], h[2], fc[20], f[30], fc[30]);
full_adder F32(f[23], fc[22], hc[2], f[31], fc[31]);
full_adder F33(f[24], fc[23], pp[6][4], f[32], fc[32]);
full_adder F34(f[15], fc[14], fc[25], f[33], fc[33]);


//fourth level
half_adder H5(f[27], hc[3], h[4], hc[4]);
full_adder F35(f[18], fc[17], fc[27], f[34], fc[34]);
half_adder H6(f[28], pp[6][0], h[5], hc[5]);
half_adder H7(f[29], fc[28], h[6], hc[6]);
full_adder F36(f[30], fc[29], fc[21], f[35], fc[35]);
full_adder F37(f[31], fc[30], fc[10], f[36], fc[36]);
full_adder F38(f[32], fc[31], pp[7][3], f[37], fc[37]);
full_adder F39(f[25], fc[24], fc[32], f[38], fc[38]);

// last level
half_adder H8(f[34], hc[4], h[7], hc[7]);
half_adder H9(h[5], fc[34], h[8], hc[8]);
half_adder H10(h[6], hc[5], h[9], hc[9]);
half_adder H11(f[35], hc[6], h[10], hc[10]);
half_adder H12(f[36], fc[35], h[11], hc[11]);
half_adder H13(f[37], fc[36], h[12], hc[12]);
half_adder H14(f[38], fc[37], h[13], hc[13]);
half_adder H15(f[33], fc[38], h[14], hc[14]);
half_adder H16(f[26], fc[33], h[15], hc[15]);
half_adder H17(pp[7][7], fc[26], h[16], hc[16]);

always@(*)
begin
    product[0] <= pp[0][0];
    product[1] <= h[0];
    product[2] <= h[1];
    product[3] <= h[3];
    product[4] <= h[4];
    product[5] <= h[7];
    product[6] <= h[8];
    product[7] <= h[9];
    product[8] <= h[10];
    product[9] <= h[11];
    product[10] <= h[12];
    product[11] <= h[13];
    product[12] <= h[14];
    product[13] <= h[15];
    product[14] <= h[16];
    product[15] <= hc[16];
end
endmodule

```

**RTL VIEW:**

 

## TESTBENCH:


## CODE SNIPPET:

```
module wallace_testbench;
reg [7:0]a;
reg [7:0]b;
wire [15:0]product;


wallace_8 DUT (.a(a),.b(b),.product(product));
initial
begin

    a = 8'd10; b = 8'd10; #50;
    a = 8'd25; b = 8'd100; #50;
    a = 8'd5; b = 8'd5; #50;
    a = 8'd64; b = 8'd69; #100;
    a = 8'd15; b = 8'd5; #100;
    a = 8'd99; b = 8'd10; #100;
    a = 8'd78; b = 8'd90; #100;
    a = 8'd110; b = 8'd0; #100;
    a = 8'b11111110; b = 8'b10000000; #100;
    #5 $finish;
end
endmodule
```

## Modelsim output in Decimal:

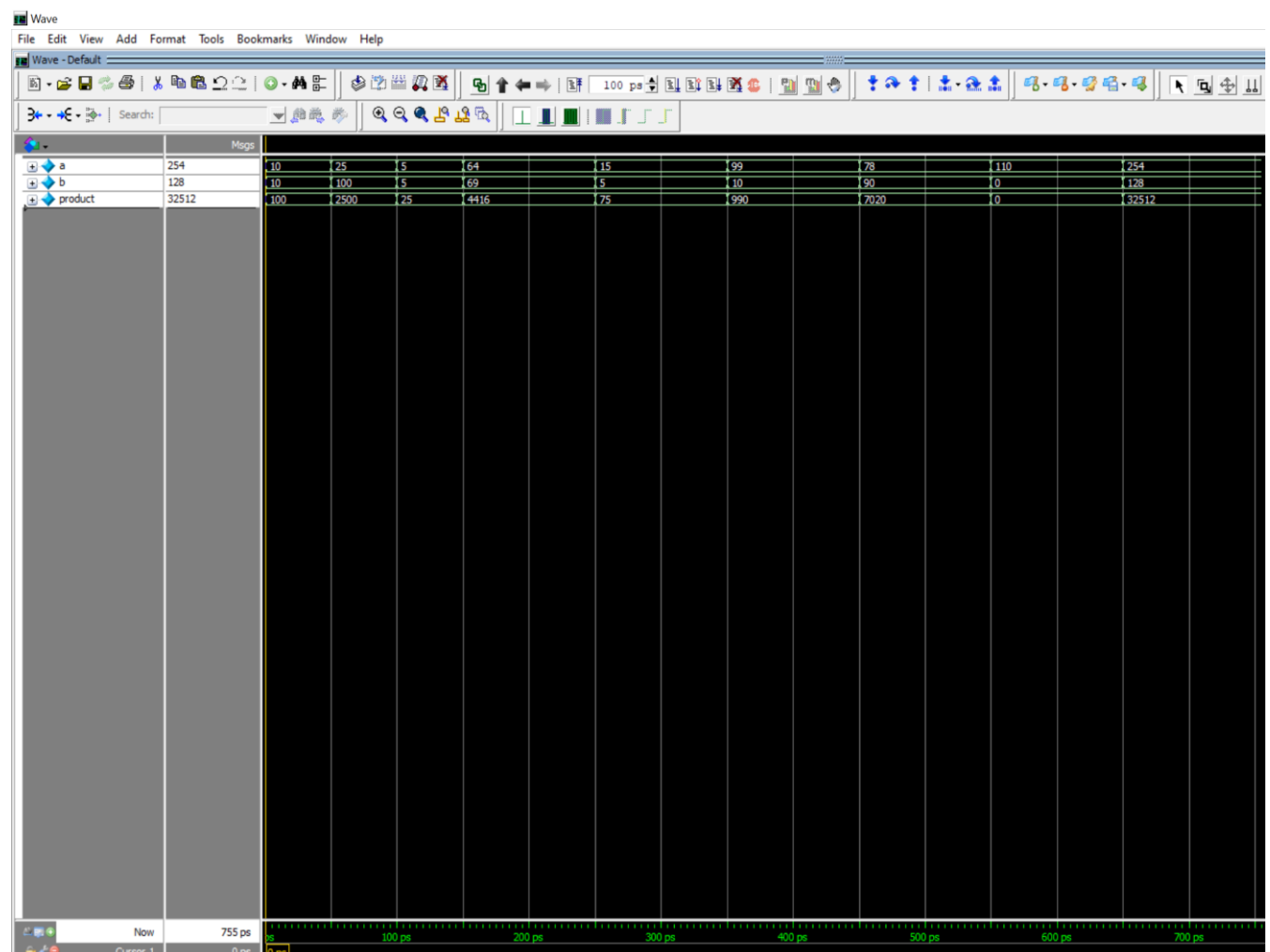

### Modelsim output in Binary:

 

### Conclusion:

From the above two waves of modelsim we can see that for multiple values of two 8-bit numbers we are getting correct product results, for Example → A = 78 & B = 90, Product = 7020. A = 110 & B = 0, Product = 0. A = 254 & B = 128, Product = 32512.

Moreover, we can see that for 8x8 bits multiplication we are getting only bits as output product and **no extra bit is being generated for carryout**, this is the special nature for modified Wallace multiplier.